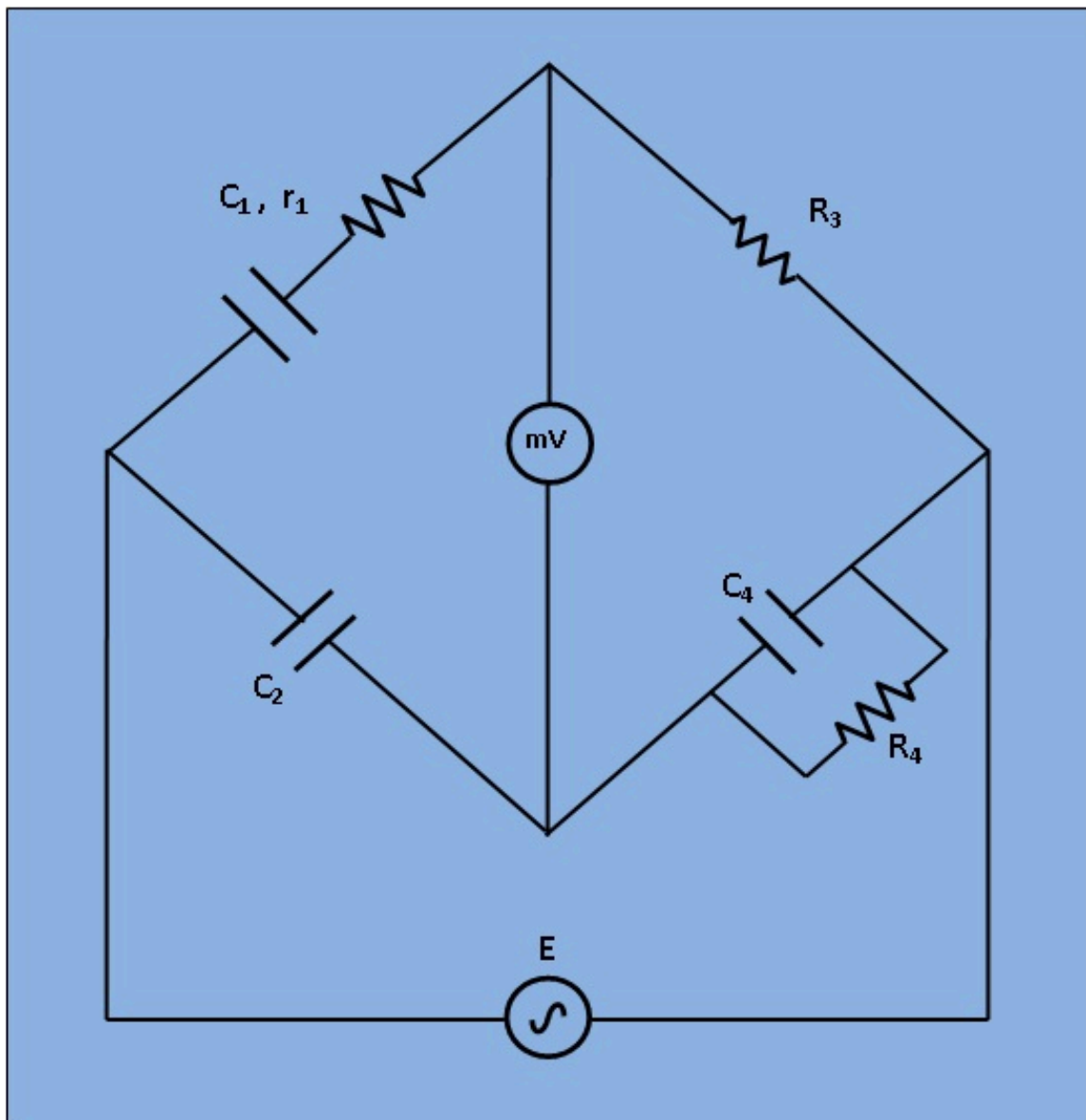


# Measurement of Capacitance by Schering Bridge

## AIM:

- To Determine the Capacitance of an unknown Capacitor.

## THEORY:



*Fig 1: Circuit diagram for measurement of Capacitance by Schering Bridge*

Let,

$C_1$ =capacitor whose capacitance is to be measured.

$r_1$ = a series resistance representing the loss in the capacitor  $C_1$ .

$C_2$ = a standard capacitor.

$R_3$ = a non inductive resistance.

$C_4$ = a variable capacitor.

$R_4$ = a variable non inductive resistance.

At balance,

$$(r_1 + \frac{1}{j\omega C_1}) * (\frac{R_4}{j\omega C_4 R_4 + 1}) = \frac{R_3}{j\omega C_2} \dots\dots (1)$$

$$r_1 R_4 - \frac{jR_4}{\omega C_1} = -\frac{jR_3}{\omega C_2} + \frac{R_3 R_4 C_4}{C_2} \dots\dots (2)$$

Or equating the real and imaginary terms in equa. (2), we obtain

$$r_1 = R_3 * \frac{C_4}{C_2} \dots\dots (3)$$


$$C_1 = R_4 * \frac{C_2}{R_3} \dots\dots (4)$$

And two independent balance equations (3) and (4) are obtained if  $C_4$  and  $R_4$  are chosen as the variable elements.

Dissipation factor

$$D_1 = \omega C_1 r_1 \dots\dots (5)$$

**PROCEDURE:**

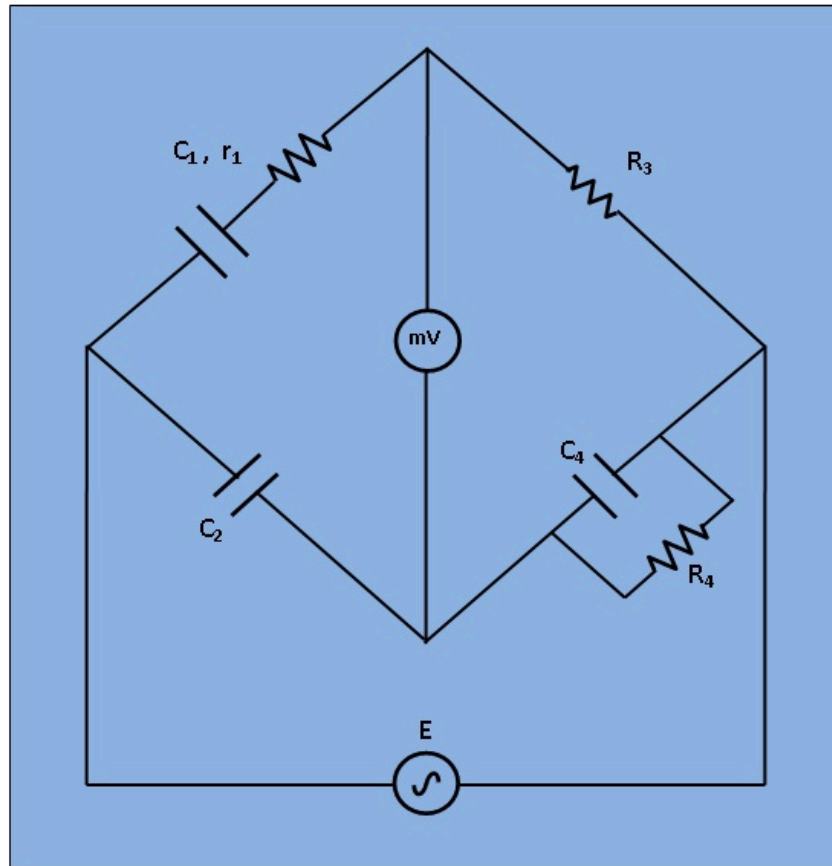


*Fig. 1. Circuit diagram of experimental set-up for Capacitance measurement by Schering Bridge.*

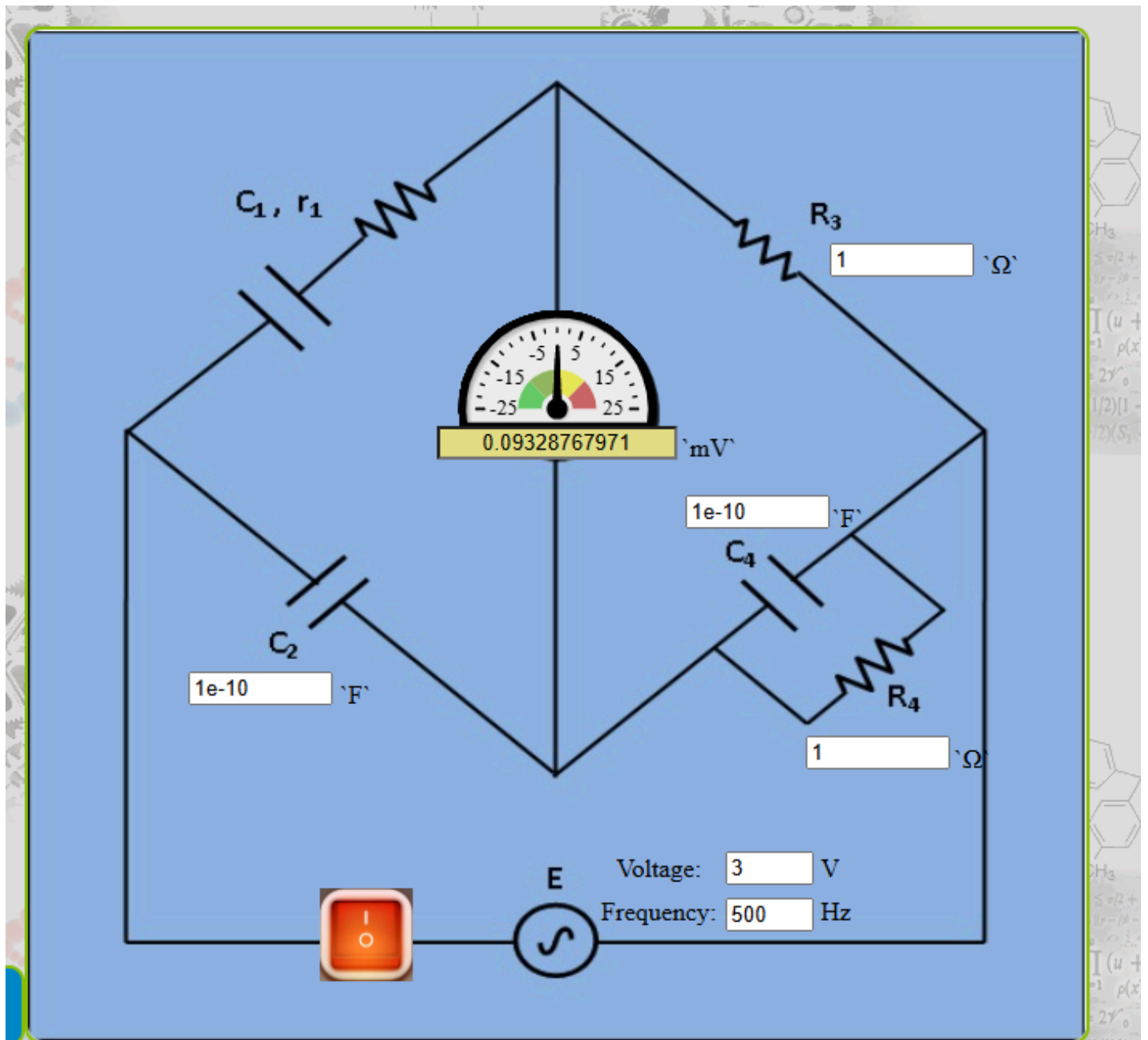- 1) Apply Supply voltage from the signal generator with arbitrary frequency. (  $V = 3V$  ). Also set the unknown Capacitance value from 'Set Capacitor Value' tab.
- 2) Then switch on the supply to get millivoltmeter deflection.
- 3) Choose the values of  $C_2$ ,  $C_4$ ,  $R_3$  and  $R_4$  from the capacitance and resistance box. Vary the values to some particular values to achieve "NULL".
- 4) Observe the millivoltmeter pointer to achieve "NULL".
- 5) If "NULL" is achieved, switch to 'Measure Capacitor Value' tab and click on 'Simulate'. Observe the calculated values of unknown capacitance ( $C_1$ ) and its internal resistance ( $r_1$ ).
- 6) Also observe the Dissipation factor of the unknown capacitor which is defined as

$$\omega * C * r \text{ Where, } \omega = 2\pi f$$

**OBSERVATION:**



The current voltmeter reading is: 0.0932876797 mv. Now simulate to get:

Capacitor value (in uF): 0.00010000

Resistance value (in Ω): 1.0000

Dissipation Factor: 3.1400e-7

Simulate

**CONTROLS**

|             |  |             |
|-------------|--|-------------|
| R3 : 1 Ω    | <div style="width: 100%; height: 10px; background: linear-gradient(to right, blue, white);"></div> | 11.11111 MΩ |
| R4 : 1 Ω    | <div style="width: 100%; height: 10px; background: linear-gradient(to right, blue, white);"></div> | 11.11111 MΩ |
| C2 : 100 pF | <div style="width: 100%; height: 10px; background: linear-gradient(to right, blue, white);"></div> | 11.111uF    |
| C4 : 100 pF | <div style="width: 100%; height: 10px; background: linear-gradient(to right, blue, white);"></div> | 11.111uF    |

## RESULT:

Thus, the unknown capacitance value is determined using Schering Bridge.